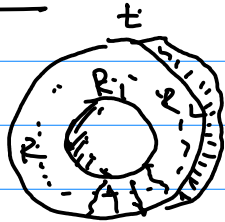


2.1.10



$$R = ? \quad I = \frac{U}{R}$$

$$\vec{j} = \sigma \cdot \vec{E}$$

$$\nabla \cdot \vec{j} = 0 = \sigma \nabla \cdot \vec{E} = \sigma \Delta \varphi = 0$$

(GAUSS) ANALOGIE - ELSTAT. - VA'LCOVY' KONDENZATOR

$$E = \frac{1}{4\pi\epsilon_0} \frac{Q}{r^2}$$

$$\varphi = \int \frac{Q}{4\pi r^2} dr$$

$$E \sim \frac{1}{r} \quad E = \frac{Q}{\lambda}$$

$$I = \int_{\sigma R} \vec{j} \cdot d\vec{S} = j \cdot 2\pi R \cdot l$$

$$= \sigma \frac{Q}{R} \cdot 2\pi R l$$

$$U = Q \cdot \ln \frac{R_2}{R_1}$$


$$R = \frac{U}{I} = \frac{Q \cdot \ln \frac{R_2}{R_1}}{j \cdot 2\pi R l}$$

DÚ

- REŠENÍ ↑ PŘOCÍ POUŽE CARLO VAHODNÉ PRŮCH.

$$\left| \begin{array}{c} 0 \\ \cdot \\ 1 \end{array} \right| \quad \varphi(r) = \int \frac{Q}{r^2} dr \text{ kde } r = "1"$$

5.1.11

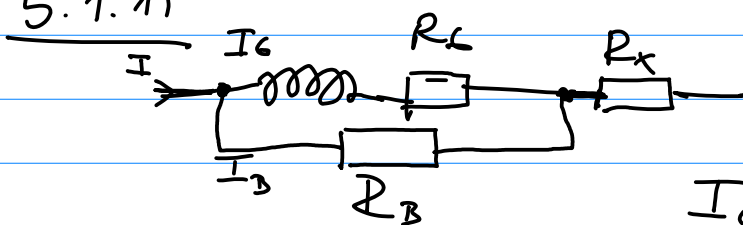

10x SNIŽIT' CITLIVOST

$$I_C = \frac{I}{10} = \frac{I_C + I_B}{10}$$

$$9 I_C = I_B$$

$$R_6 I_6 = R_3 \cdot I_3$$

$$R_B = \frac{1}{9} R_G$$



$$\frac{1}{\frac{1}{R_6} + \frac{1}{R_B}} + R_X = R_G$$

$$\frac{1}{\frac{1}{R_6} + \frac{9}{R_G}} + R_X = R_G$$


$$R_X = \frac{9}{10} R_G$$

5.1.33

THOMSONŮV PŮSTĚK

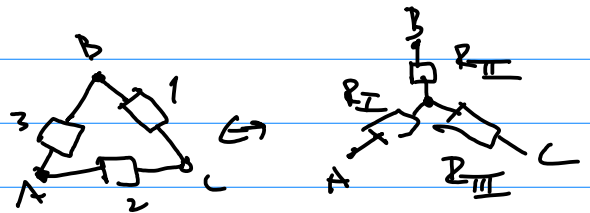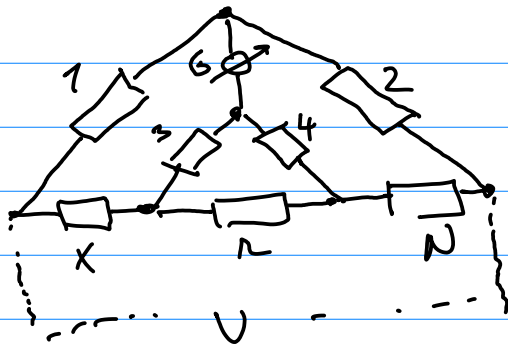
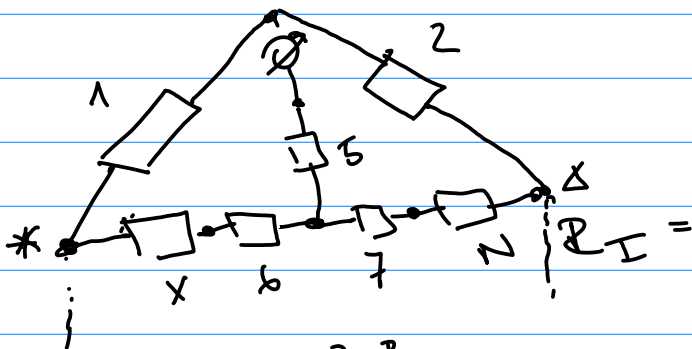
$$\frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{R_3}} = R_I + R_{II}$$



$$\frac{R_1 R_3 + R_2 R_3}{R_1 + R_2 + R_3} = R_I + R_{II}$$

$$R_I = \frac{R_3 R_2}{R_1 + R_2 + R_3}$$


$$R_5 = \frac{R_3 R_4}{R_3 + R_4 + R}$$

$$R_6 = \frac{R_3 R}{\Sigma}$$

$$R_7 = \frac{R R_4}{\Sigma}$$

WHEATSTONEŮV PŮSTĚK



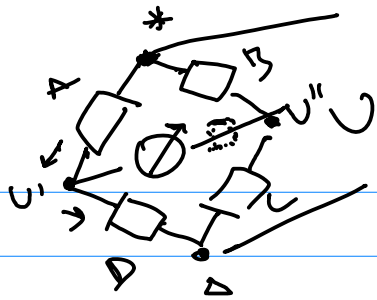

$$I_A = I_D$$

$$I_B = I_C$$

$$R_A \cdot I_A = R_D \cdot I_D$$

$$R_B \cdot I_B = R_C \cdot I_C$$

$$\frac{R_A}{R_D} = \frac{R_B}{R_C}$$

$$\frac{R_x + R_6}{R_7 + N} = \frac{R_1}{R_2}$$

$$a) \frac{R_1}{R_2} = \frac{R_x + \frac{R_3 \cdot n}{R_3 + R_4 + n}}{R_N + \frac{R_4 \cdot n}{R_3 + R_4 + n}}$$



$$b) n \rightarrow 0 \quad \frac{R_1}{R_2} = \frac{R_x}{R_N}$$

$$c) R_1 = 2R_3 \quad R_2 = 2R_4 \quad \frac{R_3}{R_4} = \frac{R_x + \frac{R_3 \cdot n}{R_3 + R_4 + n}}{\dots}$$

PROPORTIONALITÄT ...


$$\dots \frac{R_1}{R_2} = \frac{R_x}{R_N}$$

5.1.4

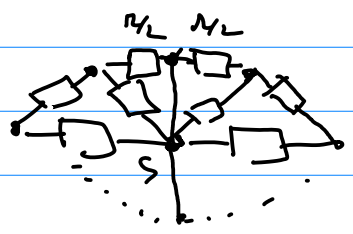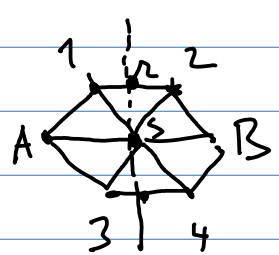

$$R_{AS} = \left(\frac{1 \cdot 2}{2 \cdot 4} + \frac{1}{n} \right)^{-1}$$

$$= \frac{2}{5} n$$

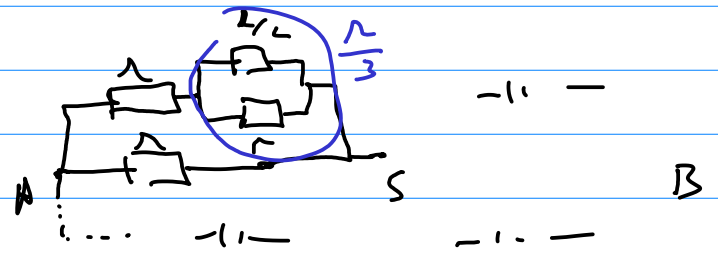

$$R = 2 \cdot R_{AS} = \frac{4}{5} n \quad (?)$$