

Cv3/2

poloměr... R

plošná hustota... σ

$\psi = \chi$

elektrický potenciál

Vně sféry: intenzita:

$$\oint \vec{E} \cdot \vec{n} ds = \frac{Q}{\epsilon_0} \quad \text{Gaussova věta}$$

$$E \cdot \underbrace{4\pi R^2}_{\text{plocha koule}} = E \cdot \underbrace{4\pi r^2}_{\text{plocha koule}} = \frac{Q}{\epsilon_0} \quad \rightarrow \quad E = \frac{Q}{4\pi r^2 \epsilon_0}$$

$$Q = S \cdot \sigma = 4\pi R^2 \sigma$$

$$E = \frac{4\pi R^2 \sigma}{4\pi r^2 \epsilon_0} = \frac{R^2 \sigma}{r^2 \epsilon_0}$$

Elektrický potenciál

$$\psi = - \int_{\infty}^r E dr = - \frac{R^2 \sigma}{\epsilon_0} \int_{\infty}^r \frac{1}{r^2} dr = - \frac{R^2 \sigma}{\epsilon_0} \left[-\frac{1}{r} \right]_{\infty}^r = \frac{R^2 \sigma}{\epsilon_0} \cdot \frac{1}{r} + \frac{R^2 \sigma}{\epsilon_0} \cdot \frac{1}{\infty} = \frac{R^2 \sigma}{\epsilon_0 r}$$


Uvnitř sféry: intenzita je nulová (není v ní žádný náboj)

Elektrický potenciál

$$\psi = - \int_{\infty}^r E dr = - \int_{\infty}^R E dr - \int_R^r E dr$$

$$\psi = - \int_{\infty}^R E dr = \frac{R^2 \sigma}{\epsilon_0} \int_{\infty}^R \frac{1}{a^2} da = \frac{R^2 \sigma}{\epsilon_0} \left[-\frac{1}{a} \right]_{\infty}^R = \frac{R^2 \sigma}{\epsilon_0 R} = \frac{R \sigma}{\epsilon_0}$$

3/5 $E = x$
náboj... Q

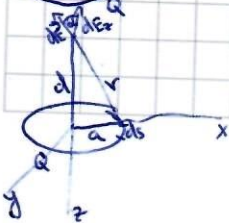


$$dE = \frac{1}{4\pi \epsilon_0} \cdot \frac{dQ}{r^2}$$

$$dE_z = dE \cdot \cos \alpha \quad \dots \quad \cos \alpha = \frac{z}{r} \quad \dots \quad r = \sqrt{R^2 + z^2} \quad \rightarrow \quad \cos \alpha = \frac{z}{\sqrt{R^2 + z^2}}$$

$$E = \frac{1}{4\pi \epsilon_0} \frac{Q}{\sqrt{R^2 + z^2}}$$

CV 34/8

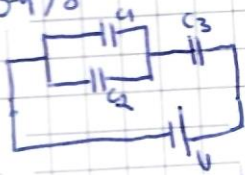

$$a) \quad C_{1,2} = \frac{C_1 + C_2}{C} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{C_1 + C_2 + C_3}{C_3 \cdot (C_1 + C_2)}$$

$$C = \frac{C_3 \cdot (C_1 + C_2)}{C_1 + C_2 + C_3}$$

$$Q = U \cdot C = \frac{U \cdot C_3 \cdot (C_1 + C_2)}{C_1 + C_2 + C_3}$$

by $Q = Q_{1,2} = Q_3$

$$Q_3 = U_3 \cdot C_3 \rightarrow U_3 = \frac{Q_3}{C_3} = \frac{Q}{C_3} = \frac{U \cdot C_3 \cdot (C_1 + C_2)}{C_1 + C_2 + C_3} = \frac{U \cdot (C_1 + C_2)}{C_1 + C_2 + C_3}$$

$$Q_{1,2} = Q_1 + Q_2$$

$$U_{1,2} = U_1 = U_2$$

$$Q_1 = U_1 \cdot C_1$$

$$Q_2 = U_2 \cdot C_2$$

$$Q_3 = \frac{U \cdot C_3 \cdot (C_1 + C_2)}{C_1 + C_2 + C_3}$$

$$U = U_{1,2} + U_3 \rightarrow U_{1,2} = U - U_3$$

$$U_{1,2} = U - \frac{U \cdot (C_1 + C_2)}{C_1 + C_2 + C_3} = \frac{U \cdot C_1 + U \cdot C_2 + U \cdot C_3 - U \cdot C_1 - U \cdot C_2}{C_1 + C_2 + C_3} = \frac{U \cdot C_3}{C_1 + C_2 + C_3} = U_1 = U_2$$

$$Q_1 = U_{1,2} \cdot C_1 = \frac{U \cdot C_3 \cdot C_1}{C_1 + C_2 + C_3}$$

$$Q_2 = U_{1,2} \cdot C_2 = \frac{U \cdot C_3 \cdot C_2}{C_1 + C_2 + C_3}$$